

# Transistors

Instructor: Morgan Redfield  
2010 February 21  
2-4:30 PM


# Today we'll be covering

- Background info about diodes
- What are transistors
- BJTs, a very common transistor
- Basic Switches
- Logic Gates
- Amplifiers

# What we won't cover

- Why transistors do what they do
- How transistors are made

# Diodes: the current valves

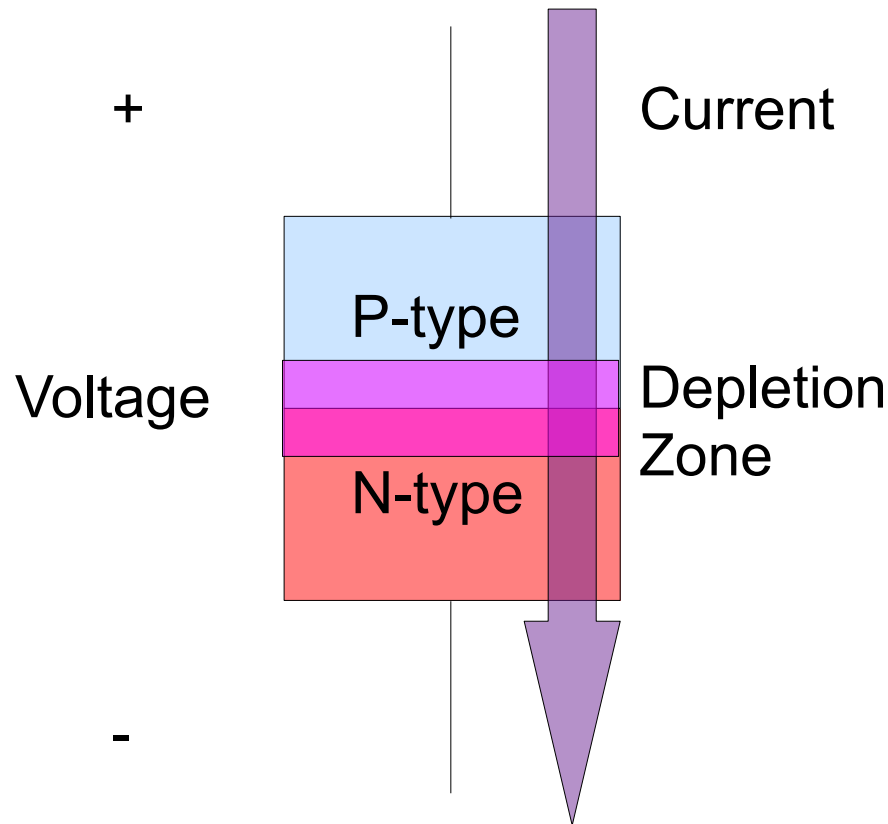

- Diodes let current through in only one direction
- They have a constant voltage drop.
- Two types of semiconductor mashed together (P-N Junction).

# What are transistors?




# What are transistors (really)?



# The semiconductor sandwich



# BJTs

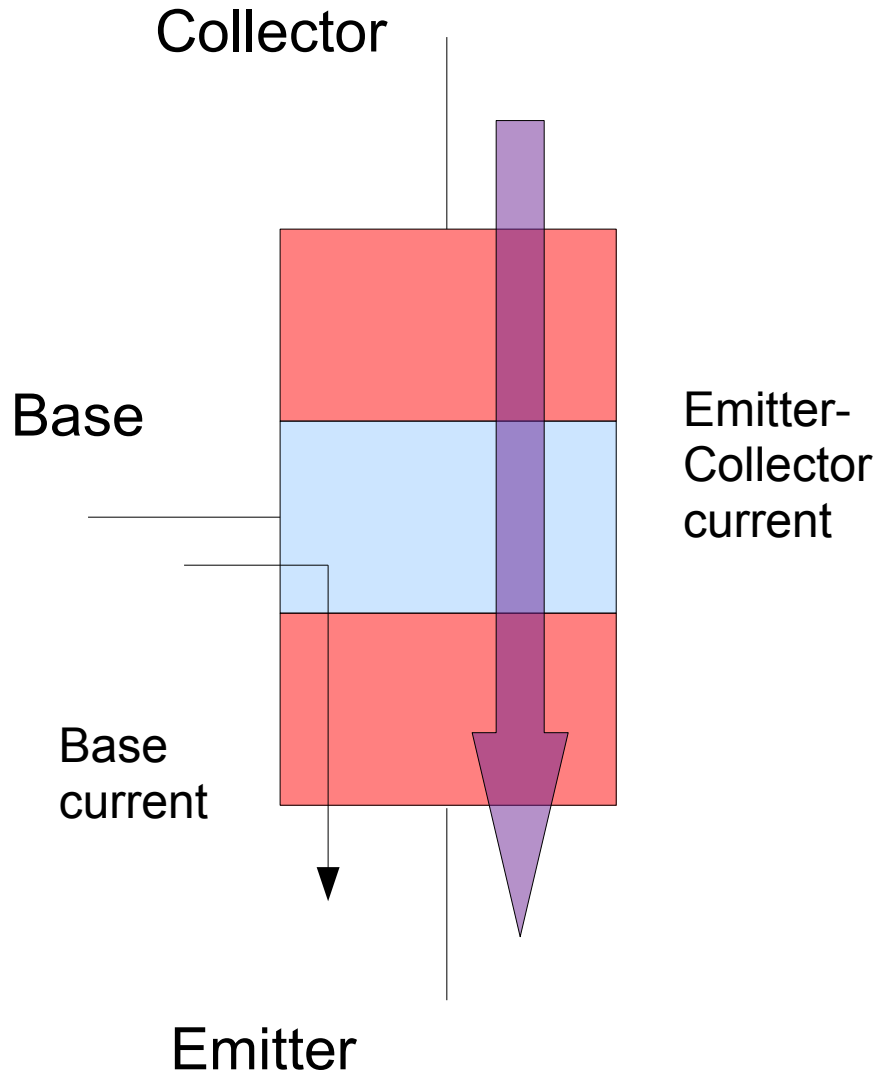

Used in:

- Very common as discrete components
- Control current
- Low voltage amplifiers
- Cheap, easy switches



# BJT

## NPN

Q1  
2N3904




## PNP

Q1  
2N3906




- Current controlled current amplifier
- Three main regions of operation
- Has current gain parameter  $\beta$


# Basic I-V curve

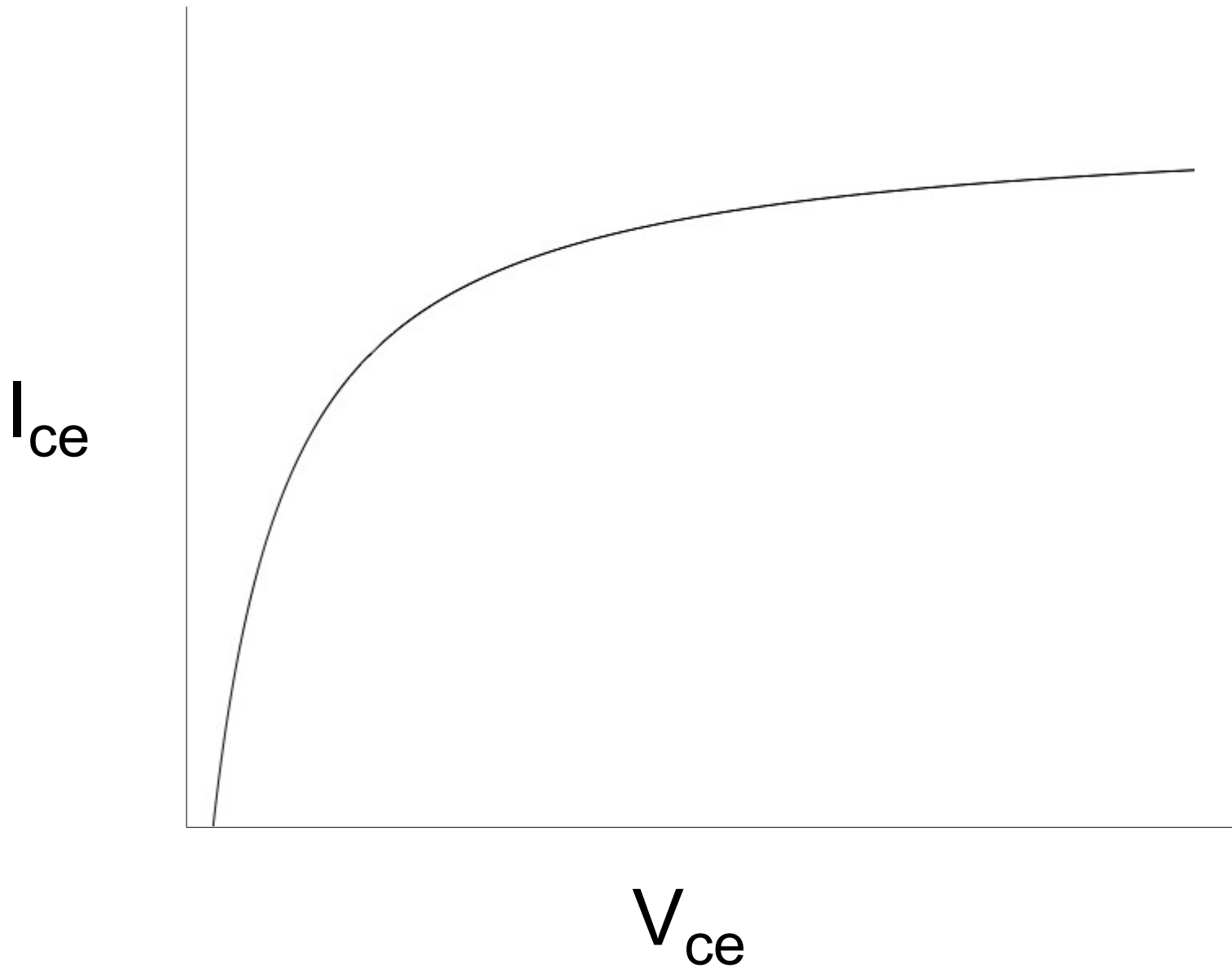

# Changing $I_{be}$ changes I-V curve

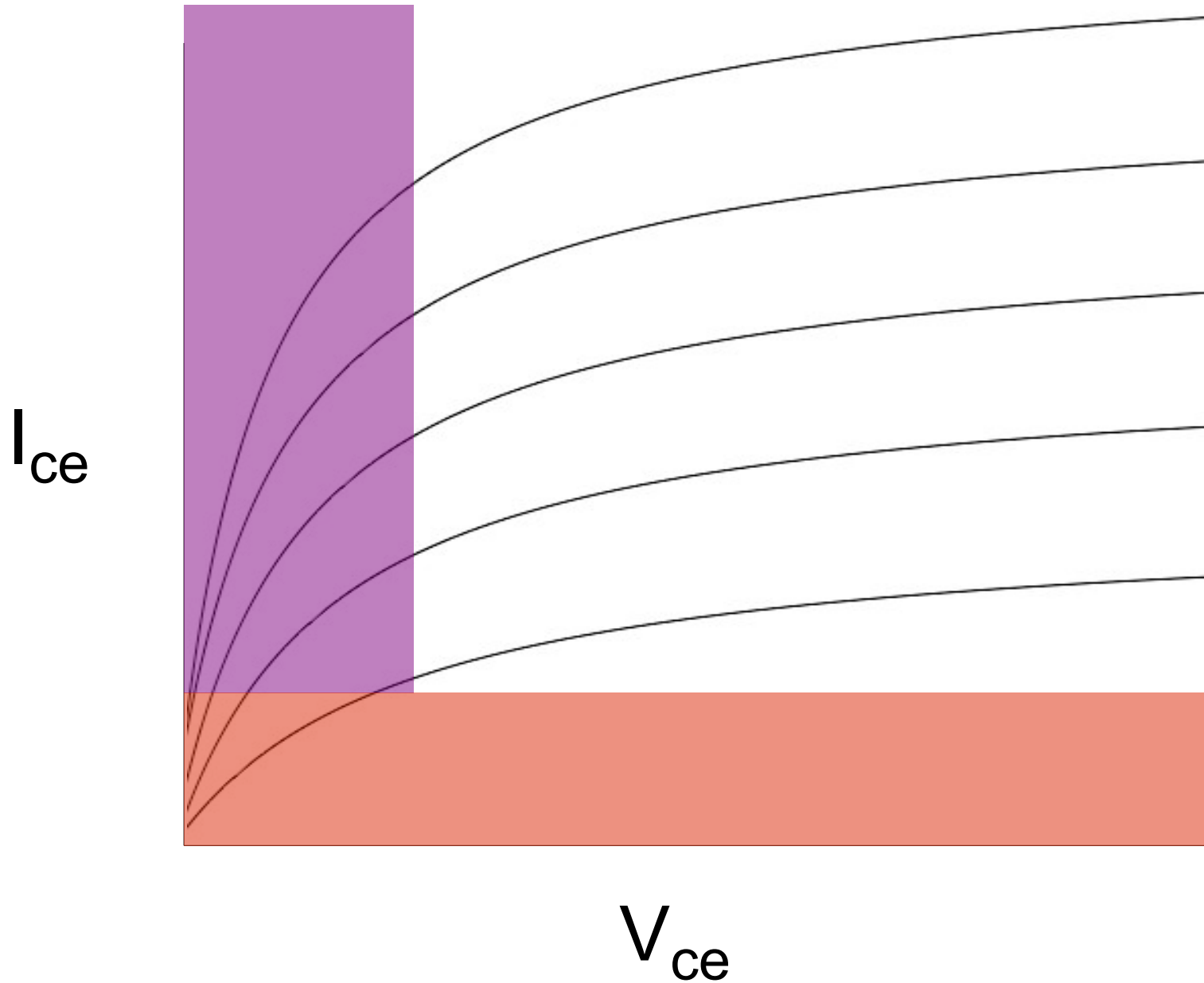


# BJT NPN regions of operation

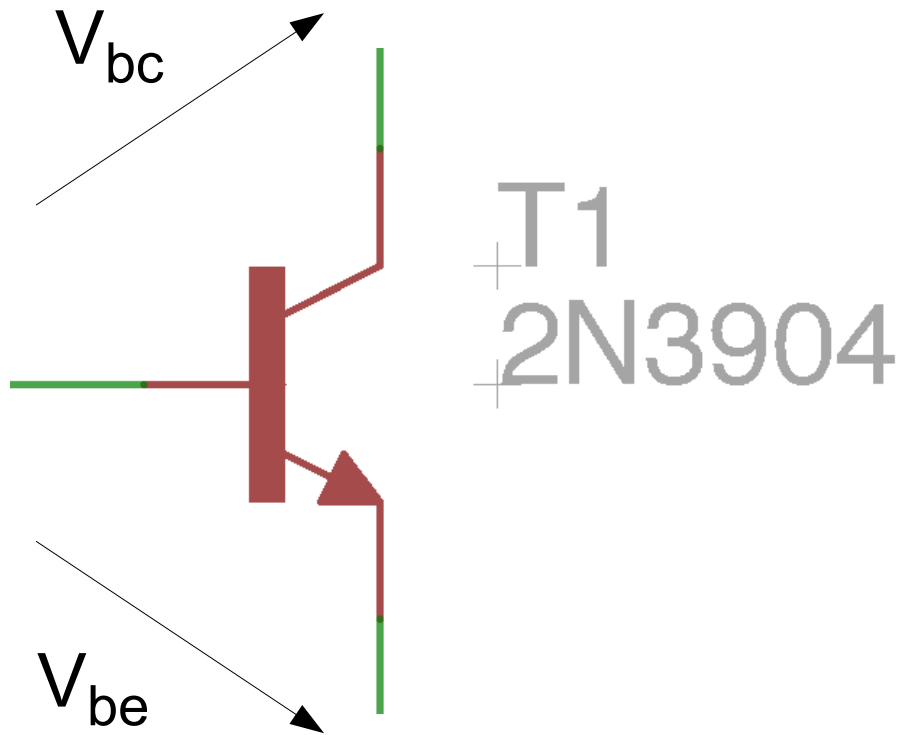


- Cut-off
  - $V_{be} < V_{th}$
  - $I_{ce} = 0$
- Forward Active
  - $V_{be} > V_{th}, V_{bc} < 0$
  - $I_{ce} = \beta_F I_{be}$
- Saturation
  - $V_{be} > V_{th}, V_{bc} > 0$
  - $I_{ce}$  depends on load

# Pull-down resistors

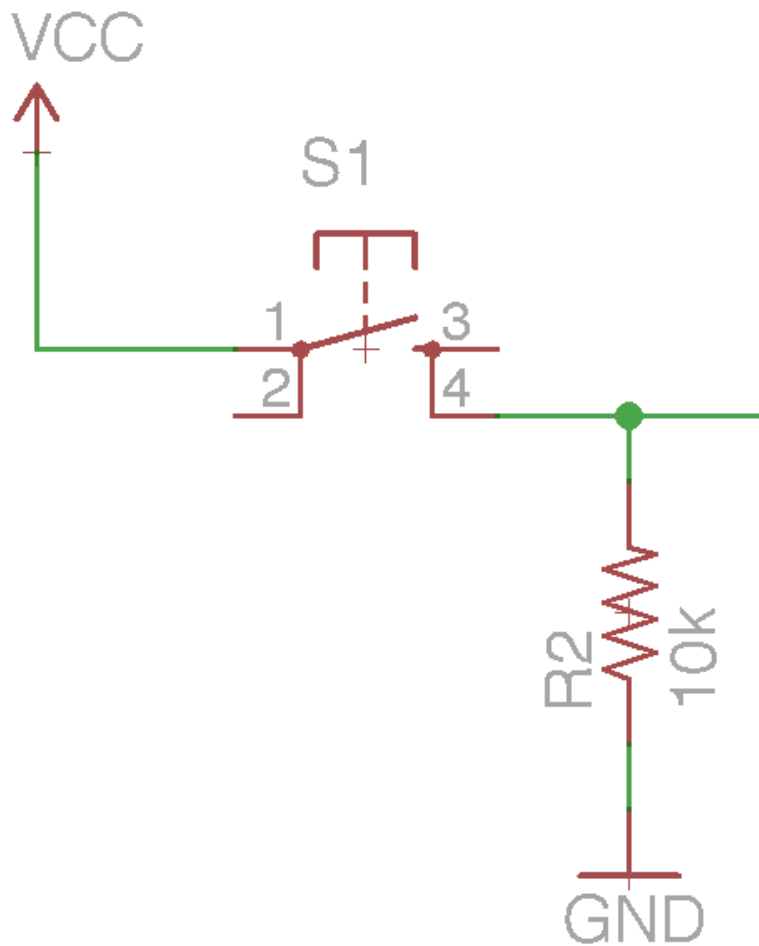


- Ensures that the input sees a certain voltage at all times
- Resistance is arbitrary
- Larger resistances are better (smaller current)

# Current limiting resistors

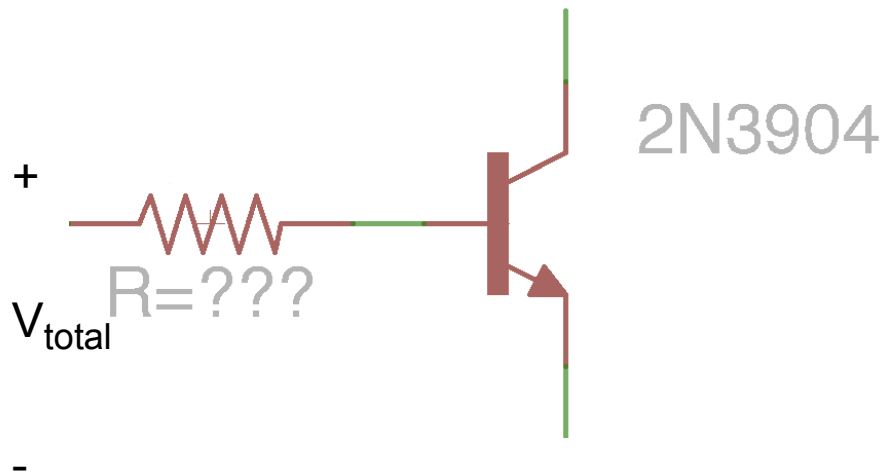


- Sets  $I_{be}$  (and thus  $I_{ce}$ )
- We know desired  $I_{ce}$ 
  - $I_{be} = I_{ce} / \beta$
- Calculate R via Ohm's Law
  - $R = V / I_{be}$
  - $V = V_{total} - V_{be}$

# The TO-92 package

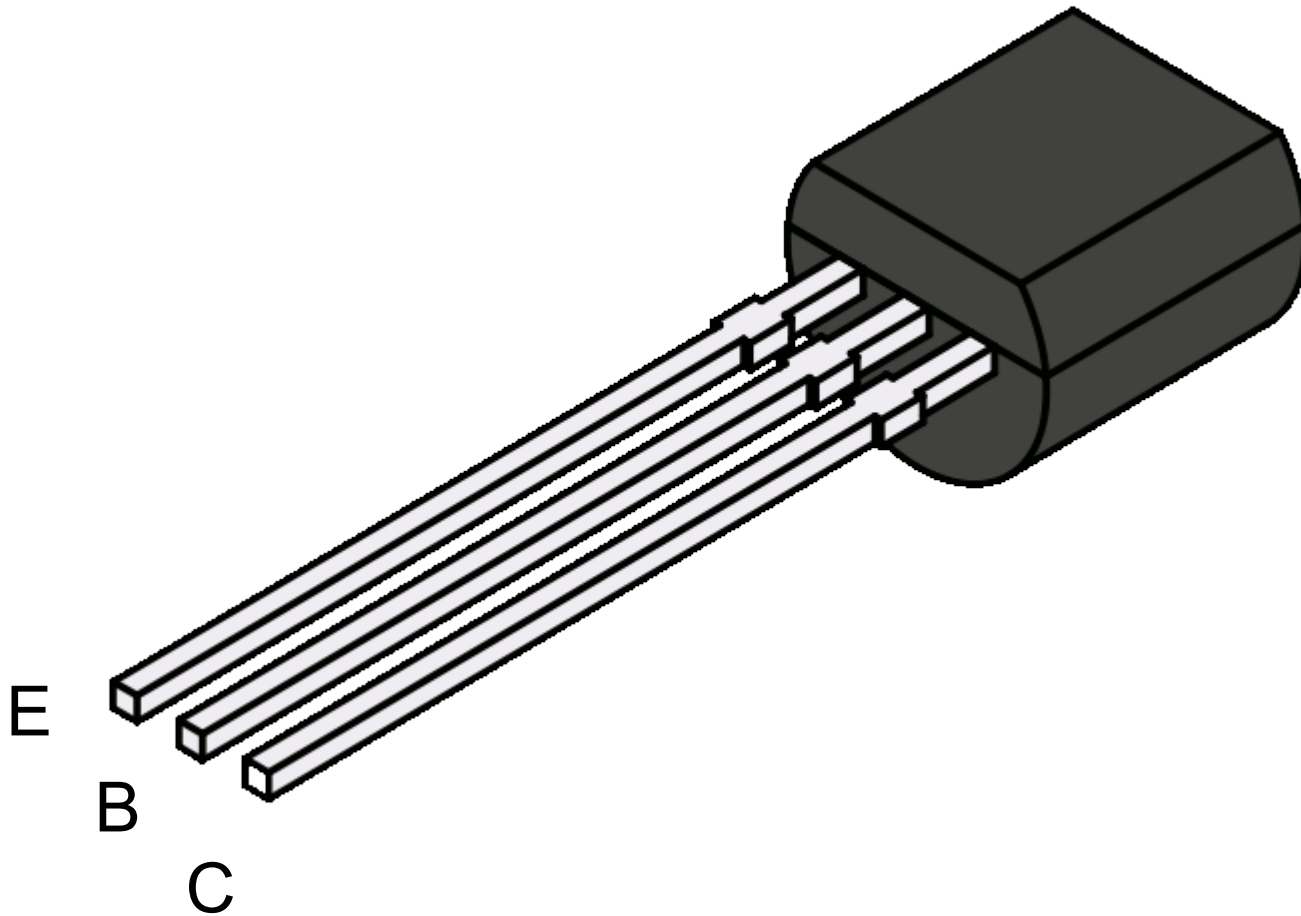


# NPN Switch

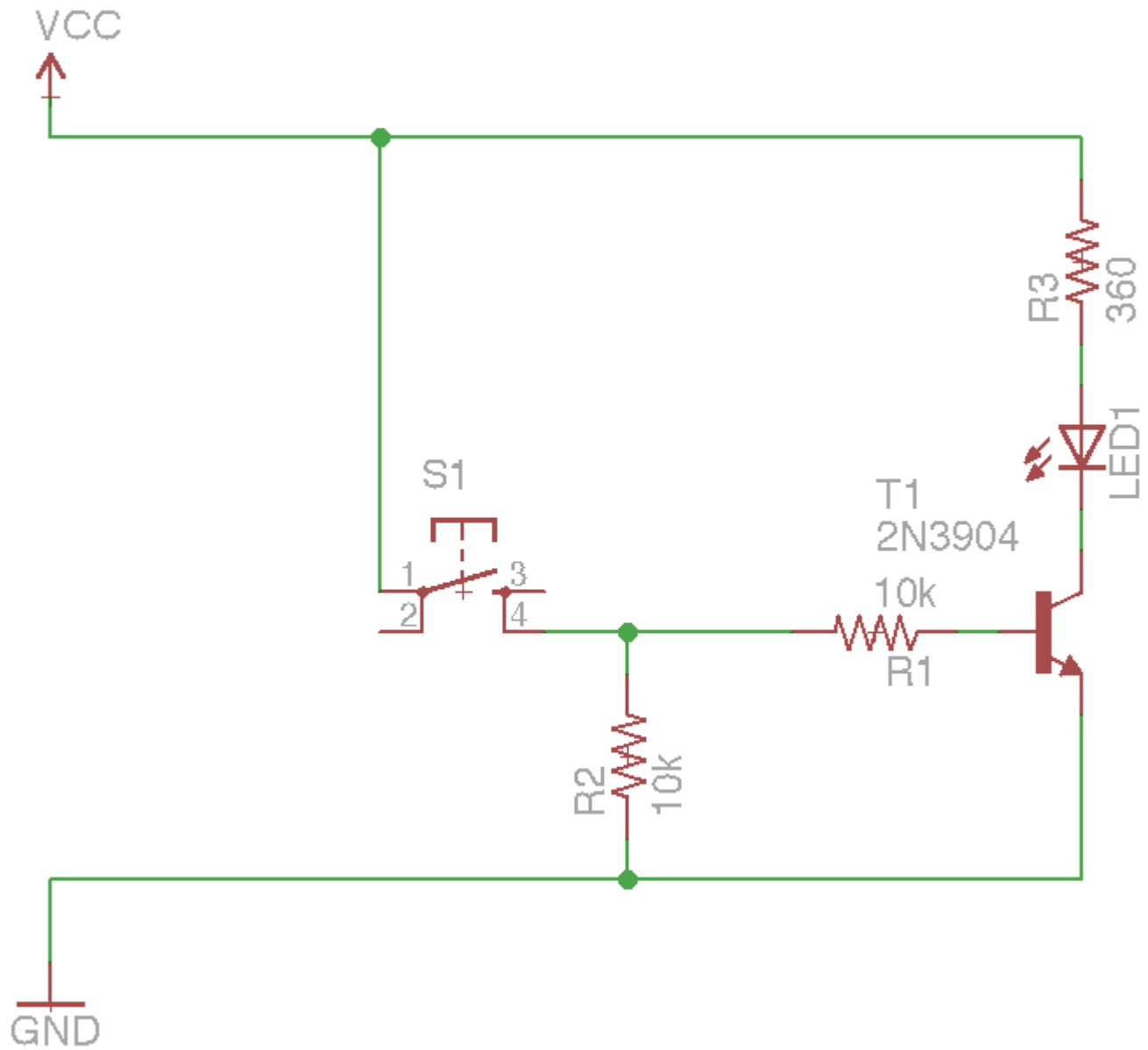




# BJT PNP regions of operation

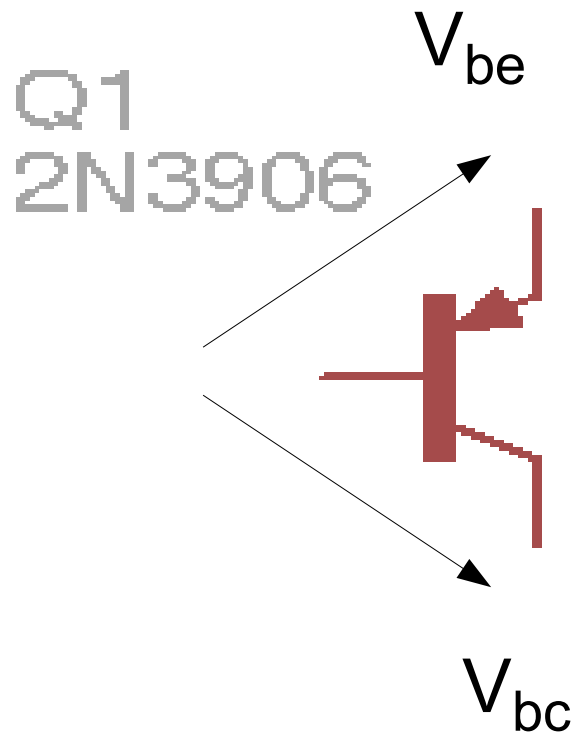


- Cut-off
  - $V_{be} > -V_{th}$ ,  $V_{bc} < 0$
  - $I_{ce} = 0$
- Forward Active
  - $V_{be} < -V_{th}$ ,  $V_{bc} > 0$
  - $I_{ce} = \beta_F I_{be}$
- Saturation
  - $V_{be} < -V_{th}$ ,  $V_{bc} > 0$
  - $I_{ce}$  depends on load

# PNP Switch

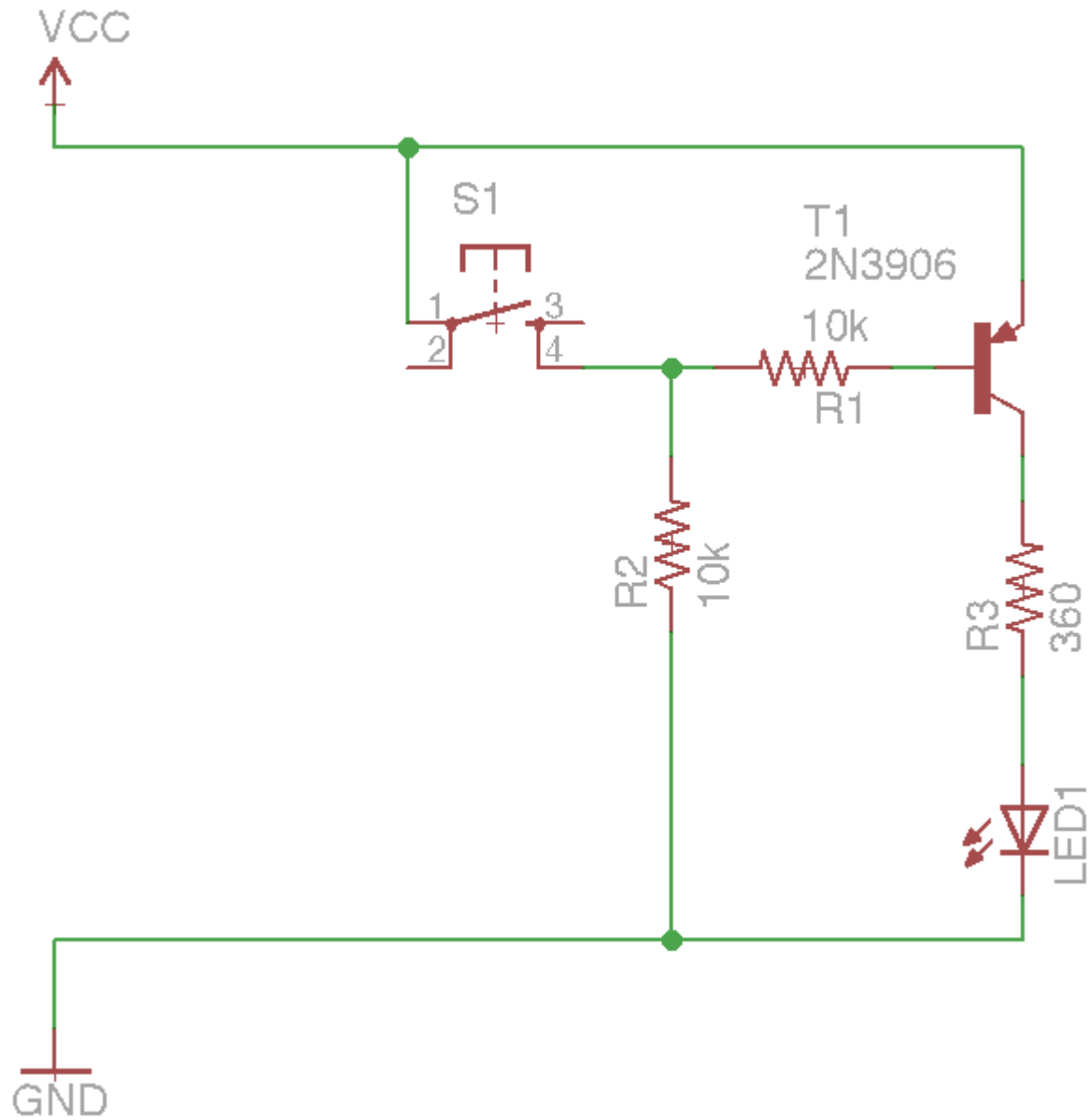


# Logic Gates


not

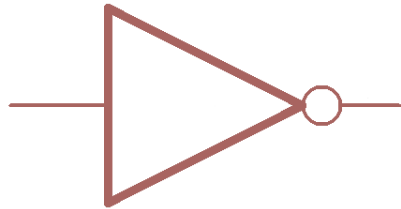

or

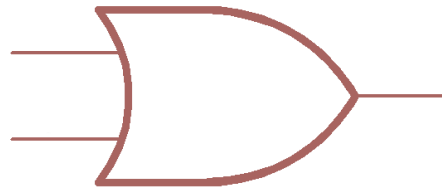


and

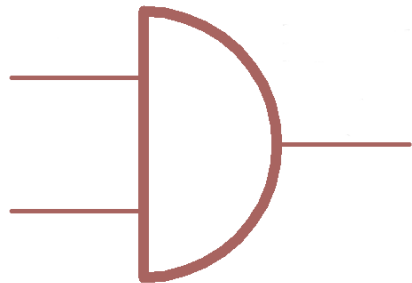


- Generate binary output from binary inputs
- Can be chained together to create complex systems
- BJT logic gates operate in the saturation and cut-off regions


# Not Gate

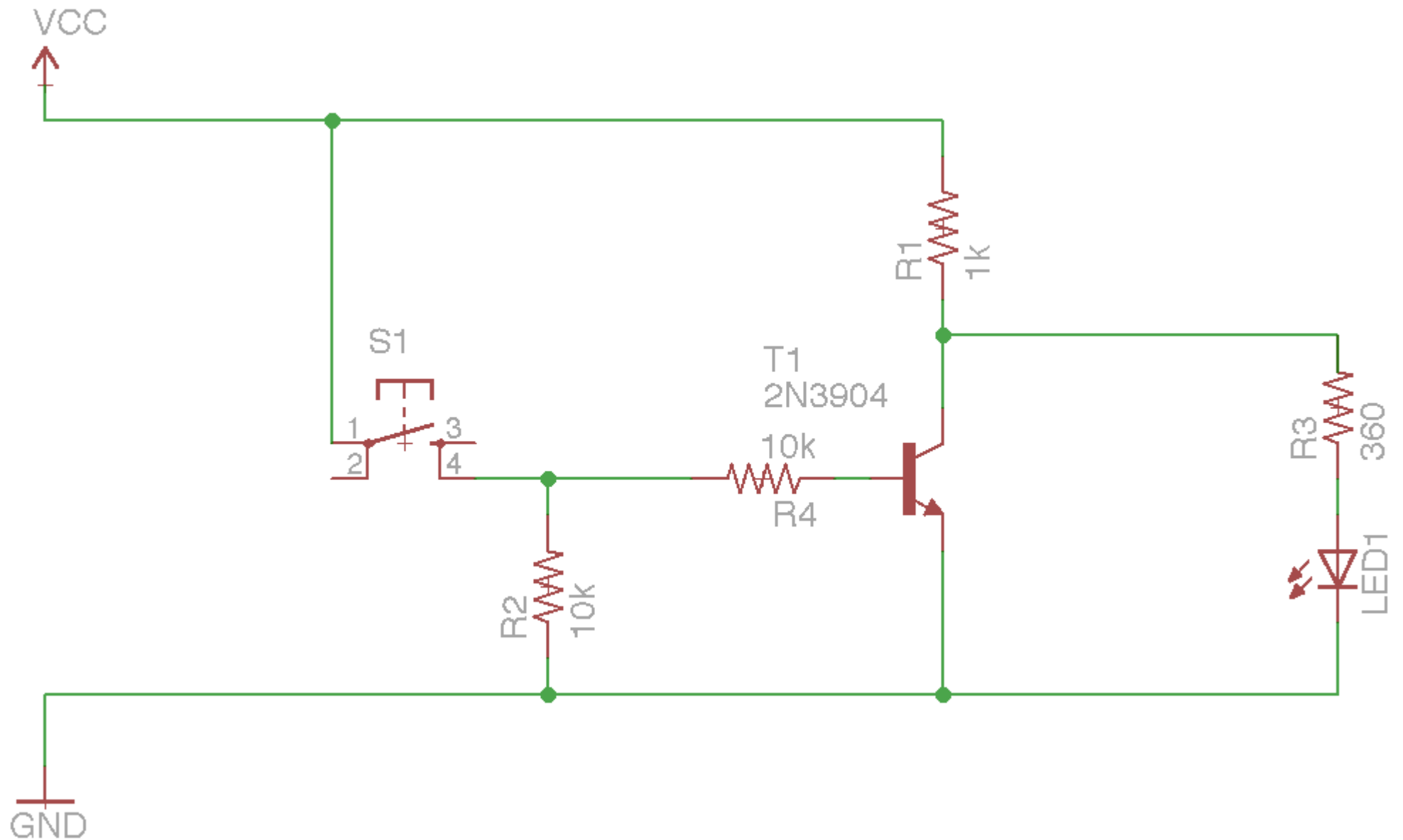


# Or Gate

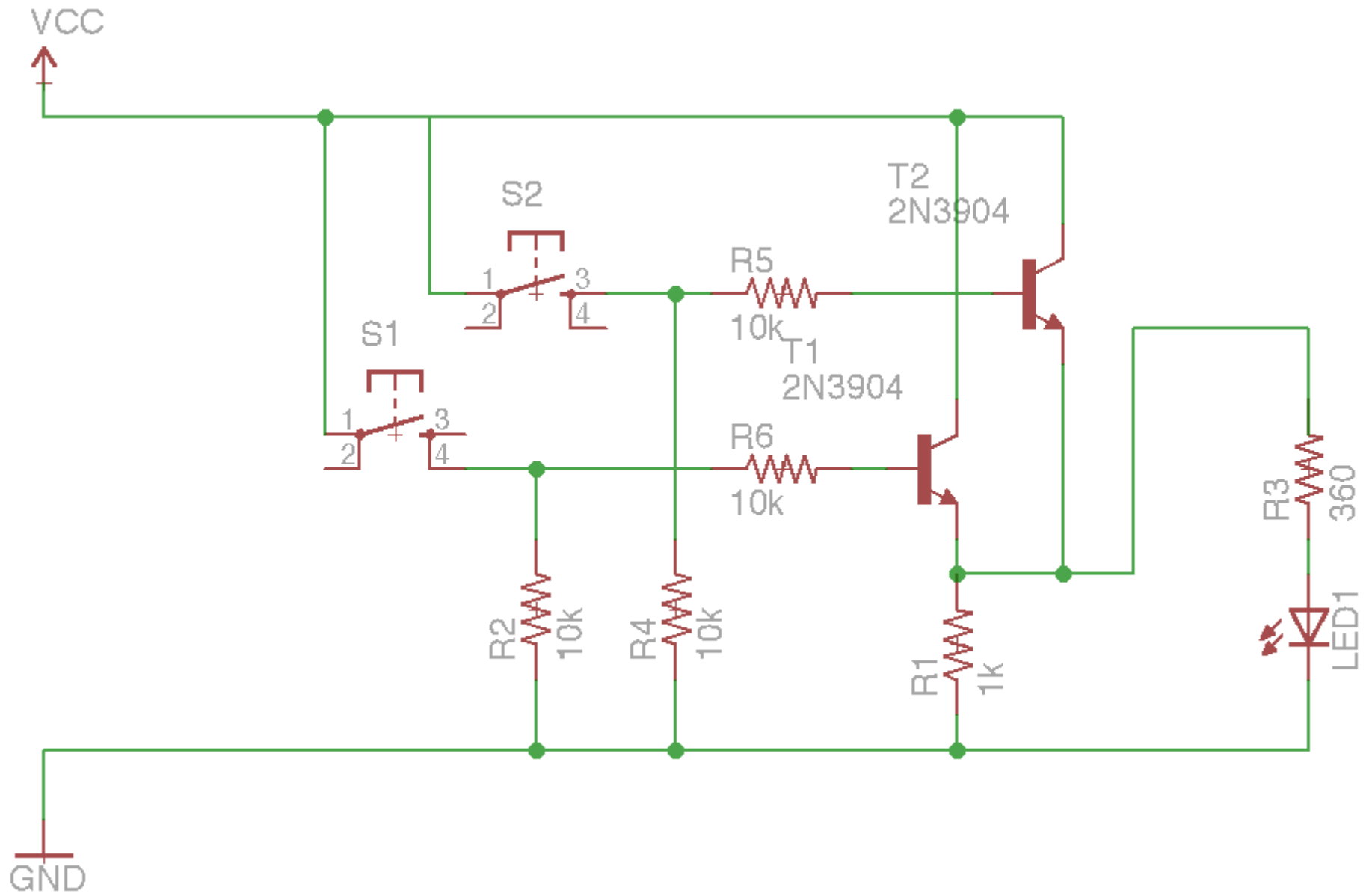

# And Gate

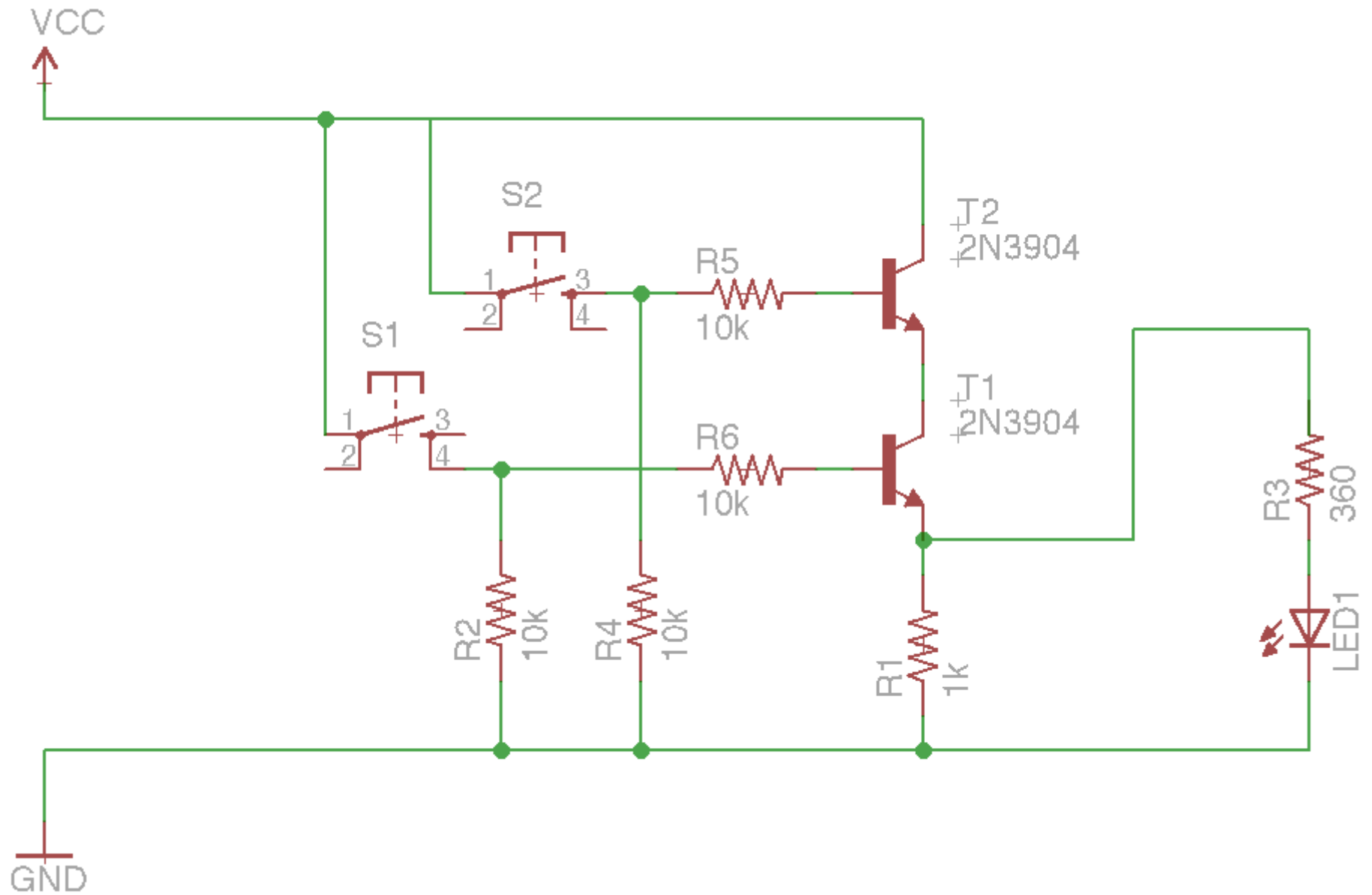


# Amplifiers

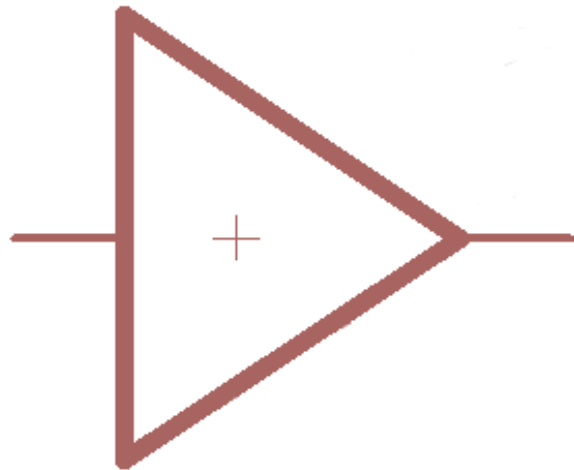

- Take a small signal and make it bigger
- Not a passive component (needs external power)
- Often used in audio, sensing, and communications

# The simplest amplifier

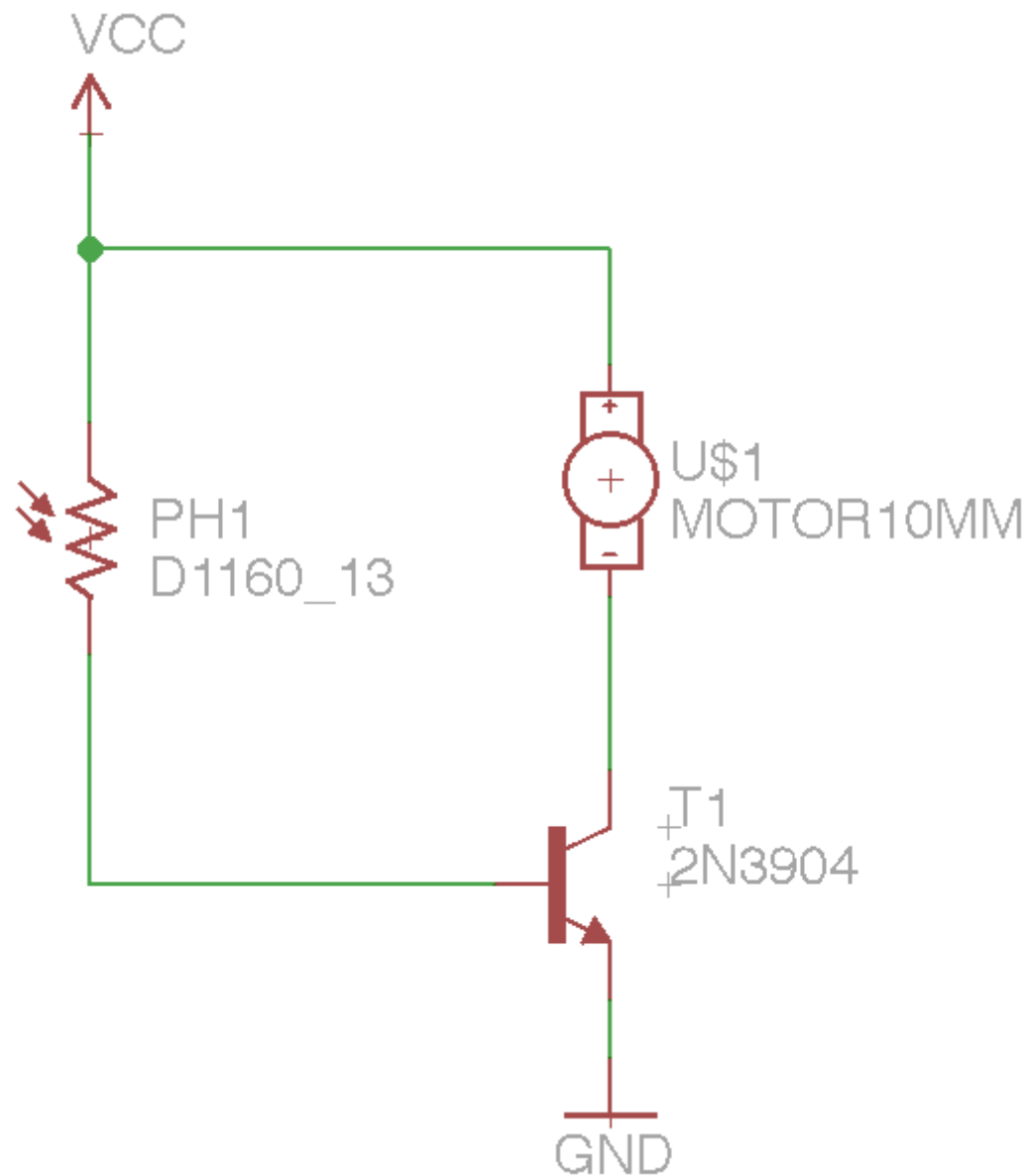



# Where do you go next?

- PSPICE
- Code, by Charles Petzold
- AC amps

# Thanks to

- Jason Zack for the switch photo on slide 4
- Matthew Bowden for the faucet photo on slide 5
- Michael Frey for the TO-92 graphic on slide 14